
ECE317: Lab 6

*Closed Loop Feedback System Design: Design of
an effective feedback compensator for a closed
loop dc-to-dc converter system*

PORLAND STATE UNIVERSITY
MASEEH COLLEGE OF ENGINEERING & COMPUTER SCIENCE
DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Authors:
STEPHEN JOHNSTON

November 22nd, 2017



ECE 317: LAB 6

CLOSED LOOP FEEDBACK SYSTEM DESIGN: DESIGN OF AN EFFECTIVE FEEDBACK COMPENSATOR FOR A CLOSED LOOP DC-TO-DC CONVERTER SYSTEM

Introduction

The objective of this lab is to design a dominant pole with lead compensator and apply it both in simulations and in real life. The compensator is composed of both a dominant pole and lead compensator, two different compensators that are handled separately. When applied, there will be significant drop in response to impedance change and in steady state error.

Compensator design

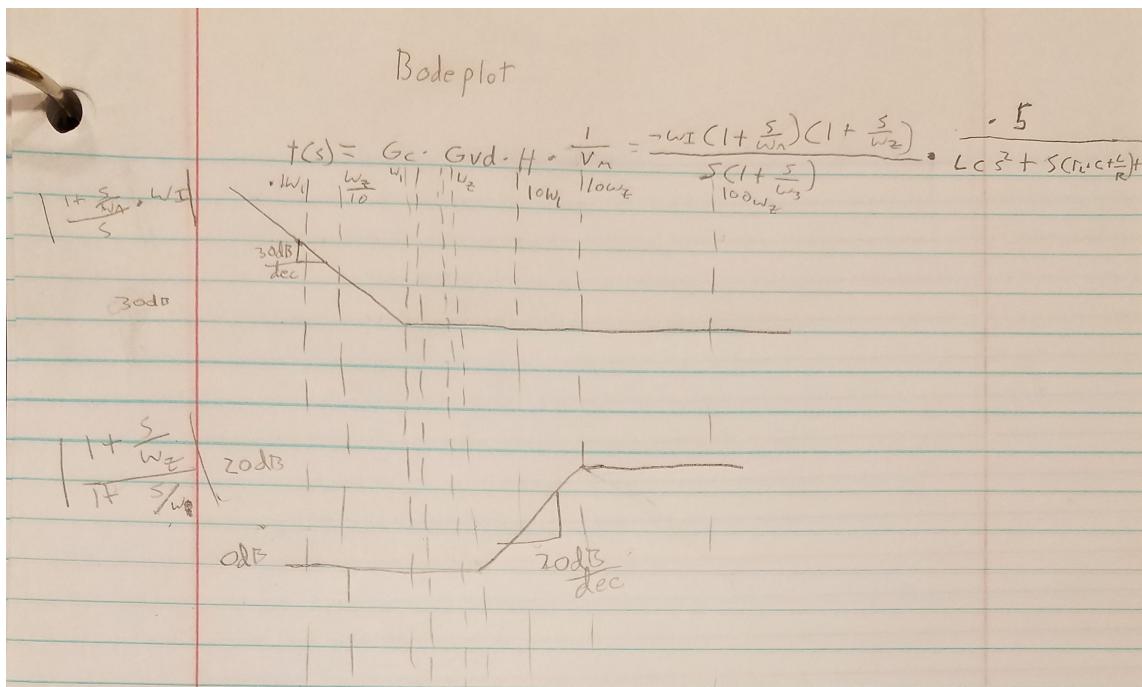


Figure 1: Compensator bode plot part 1

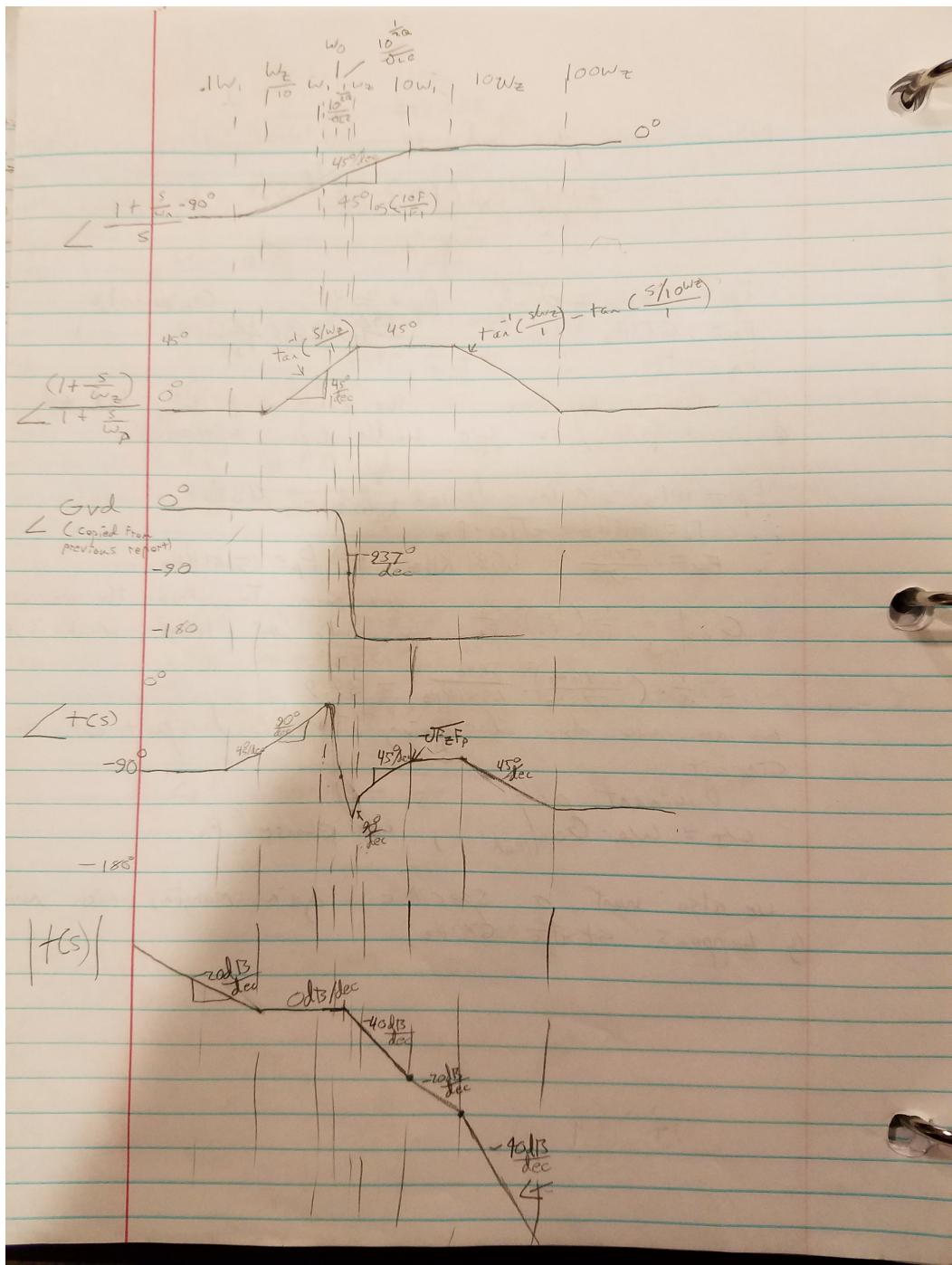


Figure 2: Compensator bode plot part 2

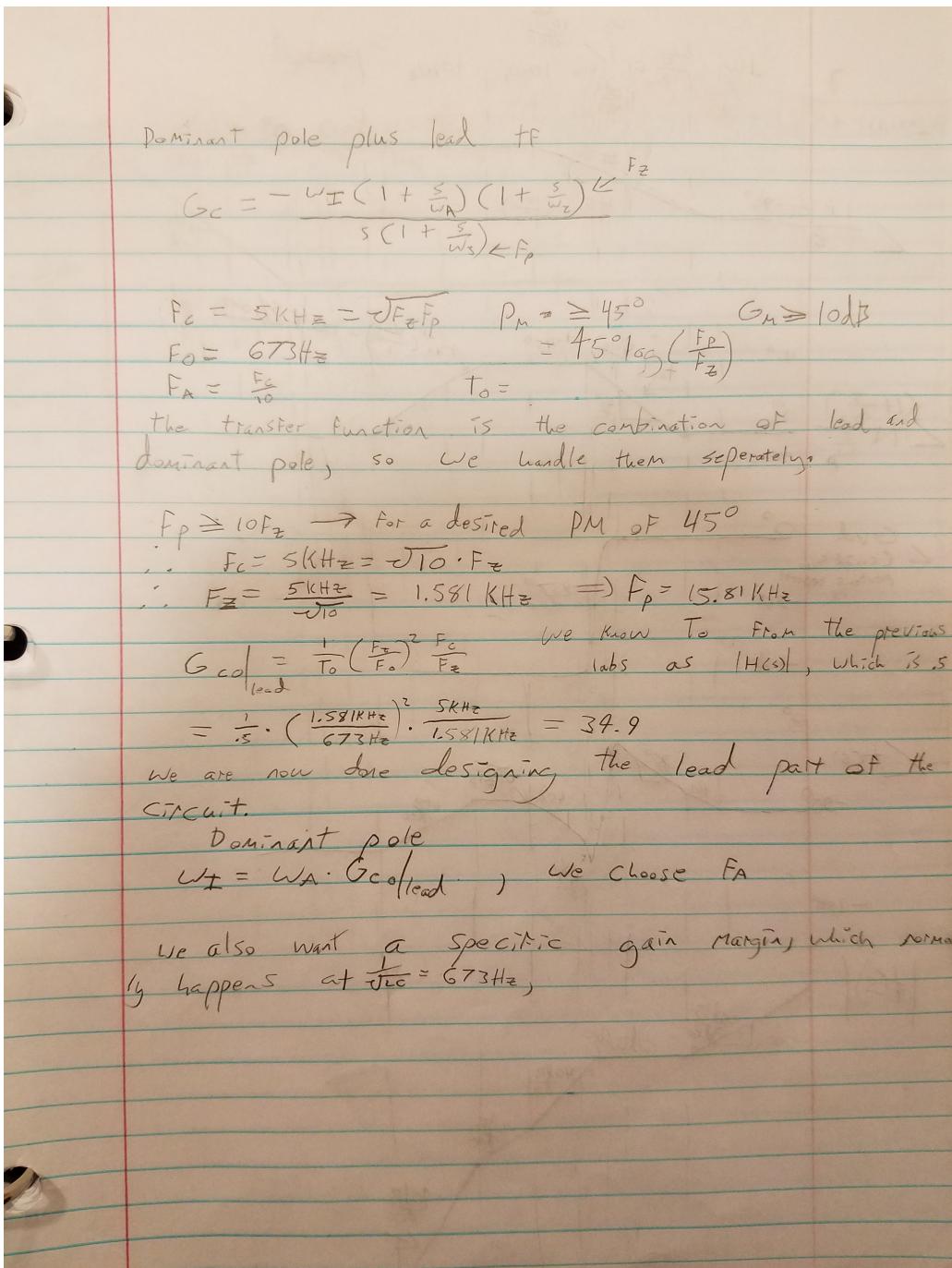


Figure 3: Circuit calculations part 1.

$$\omega_0 = \frac{1}{R_1(C_2 + C_3)} = 4228.58 \frac{\text{rad}}{\text{s}}$$

$$\omega_1 = \frac{1}{R_2 C_2} = 24.500 = 3141.59 \frac{\text{rad}}{\text{s}}$$

$$\omega_2 = \frac{1}{R_1 C_1} = 9933.71 \frac{\text{rad}}{\text{s}}$$

$$\omega_3 = \frac{1}{C_2 + C_3} = 99337.1 \frac{\text{rad}}{\text{s}}$$

$$W_{co} = \frac{1}{C_1 + C_2} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$G_{co} = 34.9$$

$$R_1 = \frac{1}{C_1 \cdot 9933.71 \frac{\text{rad}}{\text{s}}} = 100K \Rightarrow C_1 = 1nF$$

$$R_2 = \frac{1}{C_2 \cdot 3141.59 \frac{\text{rad}}{\text{s}}} = \frac{1}{C_2 \cdot 99337.1 \frac{\text{rad}}{\text{s}}} = 2.36nF$$

$$C_2 = \frac{1}{100K \cdot 4228.58} = C_3$$

$$C_2 = \frac{1}{100K \cdot 4228.58} = 2.36nF$$

$$R_2 = \frac{1}{\omega_1 C_2} = 134.877K$$

$$C_3 = \frac{1}{\omega_3 \cdot R_2 - \frac{1}{C_2}} = 77.2pF$$

$C_3 \ll C_2$
Because
 $\omega_0 \ll \omega_2$

Figure 4:Circuit calculations part 2

$C_1 = 1nf$

$C_2 = 2.34nF$

$C_3 = 77.2pF$

$R_1 = 100k\Omega$

$R_2 = 134k\Omega$

1900 SW 4th Ave, suite 60-01, Portland, OR 97201 •<https://www.pdx.edu/ece/tektronix-circuit-design-and-testing-laboratory>

MATLAB simulations

Task 2a

$$C = \frac{-\omega_I(1+\frac{s}{\omega_A})(1+\frac{s}{\omega_z})}{s(1+\frac{s}{\omega_p})}$$

$$G_{vg} = \frac{10}{LCs^2+s(R_lC+\frac{L}{R})+1+\frac{Rl}{R}}$$

$$G_l = \frac{1}{V_m} \cdot G_{vg} \cdot \frac{1}{2} \cdot C = \frac{-\omega_I(1+\frac{s}{\omega_A})(1+\frac{s}{\omega_z})}{s(1+\frac{s}{\omega_p})} \cdot \frac{10}{LCs^2+s(R_lC+\frac{L}{R})+1+\frac{Rl}{R}} \cdot \frac{1}{10} \cdot \frac{1}{2} =$$

G1 =

$$0.001757 s^2 + 22.97 s + 5.482e04$$

$$5.637e-13 s^4 + 5.646e-08 s^3 + 5.547e-05 s^2 + s$$

Matlab Loop Gain tf

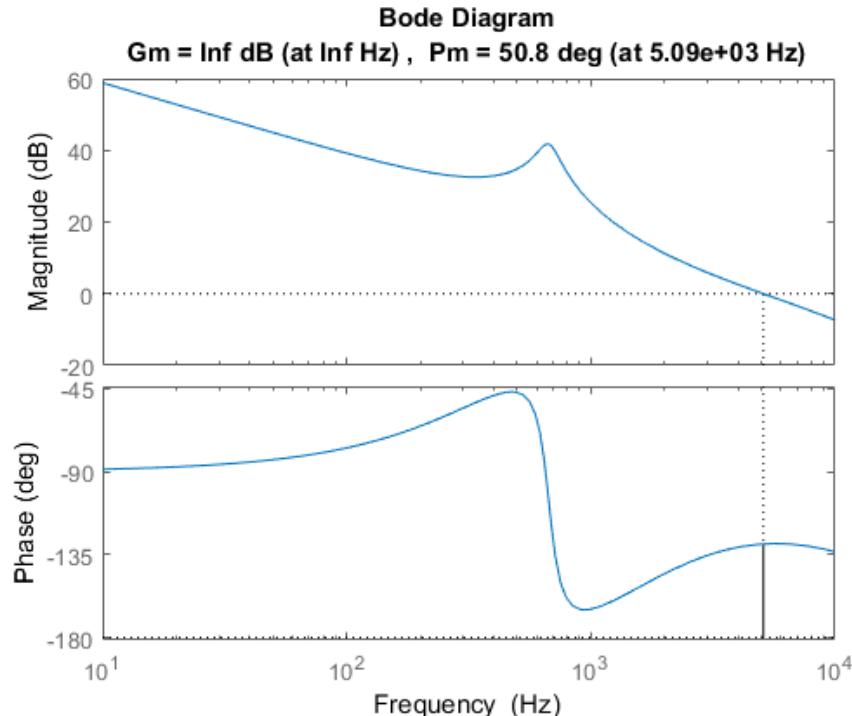


Figure 5: Bode plot of loop gain

Note the frequencies for gain margin and phase margin, inf dB at inf Hz and 50.8 degrees at 5.09kHz.

Task 2b

$$G_{cl} = 2 \cdot \frac{G_l}{1+G_l} =$$

Gcl =

$$1.981e-15 s^6 + 2.242e-10 s^5 + 2.85e-06 s^4 + 0.01225 s^3 + 52.02 s^2 + 1.096e05 s$$

$$3.178e-25 s^8 + 6.365e-20 s^7 + 4.24e-15 s^6 + 1.195e-10 s^5 + 1.541e-06 s^4 + 0.006237 s^3$$

$$+ 27.01 s^2 + 5.482e04 s$$

Closed loop expression for the transfer function

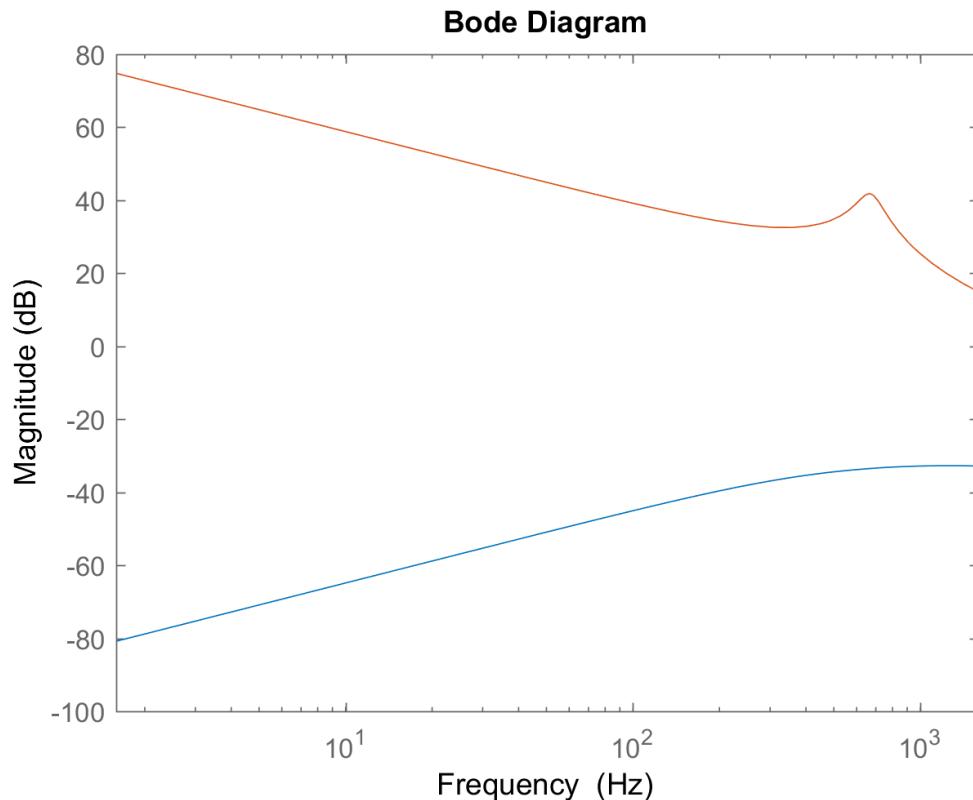


Figure 6: MATLAB Voltage closed loop and open loop plot

```

1 s = tf('s');
2 Vg = 10;
3 D = 0.5;
4 V = D*Vg;
5 L = 560*10^(-6);
6 C = 100*10^(-6);
7 R = 25;
8 R2 = 100000;
9 C2 = 22*10^-9;
10 w1 = 4226.58;
11 w2 = 3141.59;
12 w3 = 9933.7;
13 w4 = 99337.1;
14 R3 = 100000; %Given
15 C3 = 1/(w3*R3);
16 C4 = 1/(w1*R3); %Using the approximation C5 << C4
17 R4 = 1/(w2*C4);
18 C5 = 1/(w4*R4 - 1/C4);
19 vm = 10;
20 vg = 10;
21 Rl = 230*10^(-3);
22 Glpf = 1/(L*C*s^2 + s*(Rl*C + L/R) + 1); % input your loop gain
    expression as a function of s
23 Z = (L*s+Rl)*(C*s)*(1/(R))/(R + C*s*R*(L*s+Rl) + (L*s+Rl));
24 Kvd = vg;
25 H = .5;
26 K1 = 1/(R2*C2)
27 Gvd = Kvd*Glpf;
28 Gc = ((34.9*1/(R4*C4))*(1 + (s*(R4*C4)))*(1 + (s*(R3*C3))))/(s*(1+s*((R4*C5*C4)/(C5 + C4))));
29 Gpwm = 1/(vm);
30 %G_loop = Gvd*Gpwm*H*Gc;
31 Kvg = .5;
32
33 Gvg = Kvg*Glpf ; % input your expression for Gvg as a
    function of s
34 Gl = Gvd*H*(1/vm)*Gc
35 Gcl = 2*Gl/(1+Gl)
36 Gvgcl = Gvg/(1+Gl)
37 bodemag(Gl, Gcl)

```

Listing 1: Matlab Code for bodeplot of loop gain and closed loop gain

Task 2c

Zocl =

$$-3.157e-16 s^5 - 3.175e-11 s^4 - 4.405e-08 s^3 - 0.0005728 s^2 - 0.23 s$$

$$-----$$

$$3.157e-20 s^6 + 3.187e-15 s^5 + 1.046e-10 s^4 + 1.481e-06 s^3 + 0.005987 s^2 + 26.68 s + 5.533e04$$

Impedance closed loop transfer function

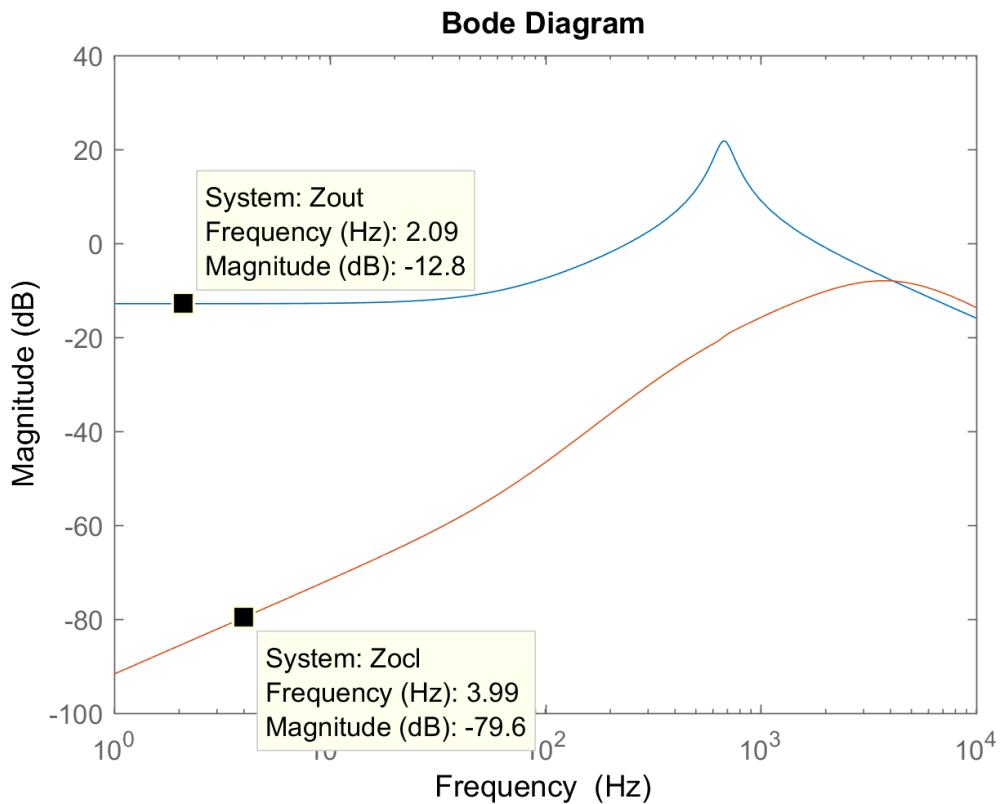


Figure 7: MATLAB impedance closed loop and open loop plots

```

1 s = tf('s');
2 Vg = 10;
3 D = 0.5;
4 V = D*Vg;
5 s = tf('s');
6 L = 560*10^(-6);
7 C = 100*10^(-6);
8 R = 25;
9
10 R2 = 100000;
11 C2 = 22*10^-9;
12 w1 = 4226.58;
13 w2 = 3141.59;
14 w3 = 9933.7;
15 w4 = 99337.1;
16 R3 = 100000; %Given
17 C3 = 1/(w3*R3);
18 C4 = 1/(w1*R3); %Using the approximation C5 << C4
19 R4 = 1/(w2*C4);
20 C5 = 1/(w4*R4 - 1/C4);
21 vm = 10;
22 vg = 10;
23 Rl = 230*10^(-3);
24 vm = 10;
25 vg = 10;
26 Rl = 230*10^(-3);
27 Glpf = 1/(L*C*s^2 + s*(Rl*C + L/R) + 1); % input your loop gain
      expression as a function of s
28 Zout = (L*s+Rl)/(1 + Rl/R + s*(L/R + Rl*C) + s^(2)*L*C);
29 Kvd = vg;
30 H = .5;
31 Gvd = Kvd*Glpf;
32
33 Gpwm = 1/(vm);
34 G_loop = Gvd*Gpwm*H;
35 Kvg = .5;
36
37 Gvg = Kvg*Glpf;
38 ; % input your expression for Zout as a function of s
39 Vg = 10;
40 D = 0.5;
41 V = D*Vg;
42 Gvg = Kvg*Glpf; % input your expression for Gvg as a
      function of s
43 Gvd = Kvd*Glpf;
44 Gc = (w1*34.9*(1 + s/(w1))*(1 + s/w2))/(s*(1 + s/w3));
45 G1 = Gvd*H*(1/vm)*Gc
46 Gcl = 2*G1/(1+G1)
47 Gvgcl = 2*Gvg/(1+G1)
48 Zocl = -Zout/(1 + G1)
49 bodemag(Zocl,Zout)

```

Listing 2: Matlab Code for bodeplot of open loop impedance and closed loop impedance
 1900 SW 4th Ave, suite 60-01, Portland, OR 97201 •
<https://www.pdx.edu/ece/tektronix-circuit-design-and-testing-laboratory>

Task 3a, Step response

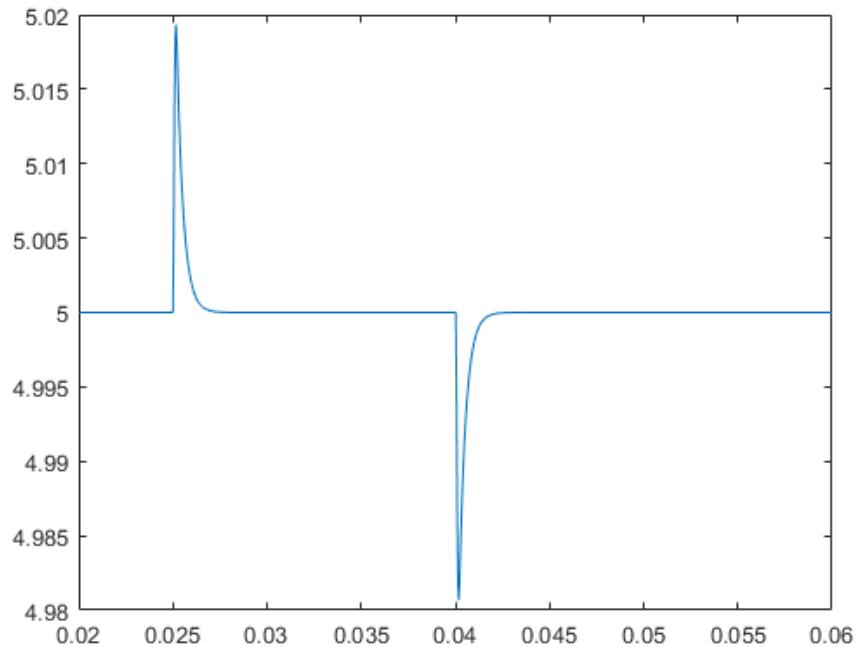


Figure 8: Voltage out step response

```
del_v =  
0.0387
```

```
SSE =  
8.8354e-18
```

```

1 s = tf('s');
2 Vg = 10;
3 D = 0.5;
4 V = D*Vg;
5 L = 560*10^(-6);
6 C = 100*10^(-6);
7 R = 25;
8 R2 = 100000;
9 C2 = 22*10^-9;
10 w1 = 4226.58;
11 w2 = 3141.59;
12 w3 = 9933.7;
13 w4 = 99337.1;
14 R3 = 100000; %Given
15 C3 = 1/(w3*R3);
16 C4 = 1/(w1*R3); %Using the approximation C5 << C4
17 R4 = 1/(w2*C4);
18 C5 = 1/(w4*R4 - 1/C4);
19 vm = 10;
20 vg = 10;
21 Rl = 230*10^(-3);
22 Glpf = 1/(L*C*s^2 + s*(Rl*C + L/R) + 1); % input your loop gain
   expression as a function of s
23 Z = (L*s+Rl)*(C*s)*(1/(R))/(R + C*s*R*(L*s+Rl) + (L*s+Rl));
24 Kvd = vg;
25 H = .5;
26 K1 = 1/(R2*C2)
27 Gvd = Kvd*Glpf;
28 Gc = ((34.9*1/(R4*C4))*(1 + (s*(R4*C4)))*(1 + (s*(R3*C3))))/(s*(1+s*((R4*C5*C4)/(C5 + C4))));
29 Gpwm = 1/(vm);
30 %G_loop = Gvd*Gpwm*H*Gc;
31 Kvg = .5;
32
33 Gvg = Kvg*Glpf ; % input your expression for Gvg as a
   function of s
34 Gl = Gvd*H*(1/vm)*Gc
35 Gcl = 2*Gl/(1+Gl)
36 Gvgcl = Gvg/(1+Gl)
37 t = linspace(0.02, 0.06, 1000);
38 u = zeros(size(t));
39 ind = find(t>=0.025 & t<=0.04);% step is between 0.025<t<0.04
40 Vg_diff = 1;
41 u(ind) = u(ind) + Vg_diff;% form input vector containing the step
42 figure(2)
43 y = lsim(Gvgcl, u, t); % simulate the step response
44 plot(t,y+V) % add steady state voltage to the output and plot it
45 del_v = max(y) - min(y) % peak-to-peak voltage deviation
46 SSE = y(ind(end)) % steady state error

```

Listing 3: MATLAB code for Voltage step response

1900 SW 4th Ave, suite 60-01, Portland, OR 97201 •
<https://www.pdx.edu/ece/tektronix-circuit-design-and-testing-laboratory>

Task 3b, Impedance step response

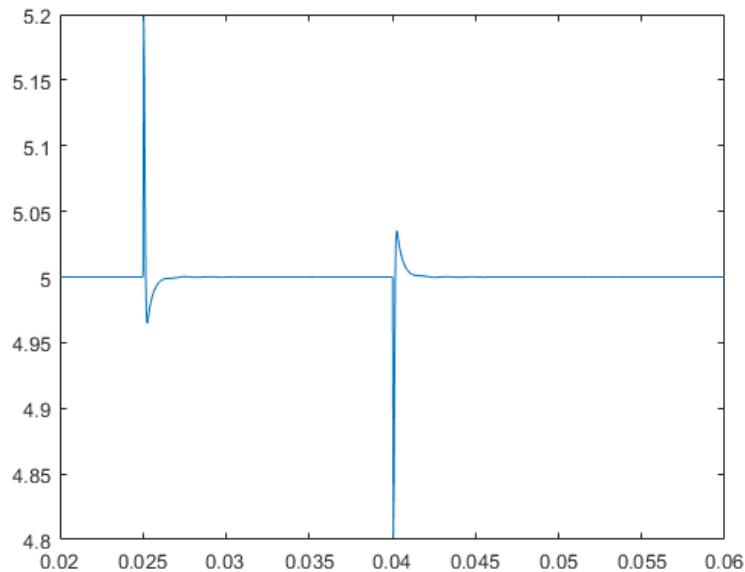


Figure 9: Impedance step response

del_v =

0.3970

SSE =

-1.1100e-06

```

1 s = tf('s');
2 Vg = 10;
3 D = 0.5;
4 V = D*Vg;
5 s = tf('s');
6 L = 560*10^(-6);
7 C = 100*10^(-6);
8 R = 25;
9
10 R2 = 100000;
11 C2 = 22*10^-9;
12 w1 = 4226.58;
13 w2 = 3141.59;
14 w3 = 9933.7;
15 w4 = 99337.1;
16 R3 = 100000; %Given
17 C3 = 1/(w3*R3);
18 C4 = 1/(w1*R3); %Using the approximation C5 << C4
19 R4 = 1/(w2*C4);
20 C5 = 1/(w4*R4 - 1/C4);
21 vm = 10;
22 vg = 10;
23 Rl = 230*10^(-3);
24 vm = 10;
25 vg = 10;
26 Rl = 230*10^(-3);
27 Glpf = 1/(L*C*s^2 + s*(Rl*C + L/R) + 1); % input your loop gain
      expression as a function of s
28 Zout = (L*s+Rl)/(1 + Rl/R + s*(L/R + Rl*C) + s^(2)*L*C);
29 Kvd = vg;
30 H = .5;
31 Gvd = Kvd*Glpf;
32
33 Gpwm = 1/(vm);
34 G_loop = Gvd*Gpwm*H;
35 Kvg = .5;
36
37 Gvg = Kvg*Glpf ;
38 ; % input your expression for Zout as a function of s
39 Vg = 10;
40 D = 0.5;
41 V = D*Vg;
42 Gvg = Kvg*Glpf ; % input your expression for Gvg as a
      function of s
43 Gvd = Kvd*Glpf;
44 Gc = (w1*34.9*(1 + s/(w1))*(1 + s/w2))/(s*(1 + s/w3));
45 Gl = Gvd*H(1/vm)*Gc
46 Gcl = 2*Gl/(1+Gl)
47 Gvgcl = 2*Gvg/(1+Gl)
48 Zocl = -Zout/(1 + Gl)
49
50 Io_1 = V/25; % load current before step. (25 ohm load)
51 Io_2 = V/5; % load current after step. (5 ohm load)
52 Io_diff = Io_2 - Io_1; % current step
53 t = linspace(0.02, 0.06, 1000);
54 u = zeros(size(t));
55 ind = find(t>=0.025 & t<=0.04); % step is between 0.025<t<0.04
56 u(ind) = u(ind) + Io_diff;
57 figure(3)
58 y = lsim(-Zocl, u, t);
59 plot(t,y+V)
60 del_v = max(y) - min(y)
61 SSE = y(ind(end))

```

Listing 4: code impedance step response

PECS simulations

Task 4a

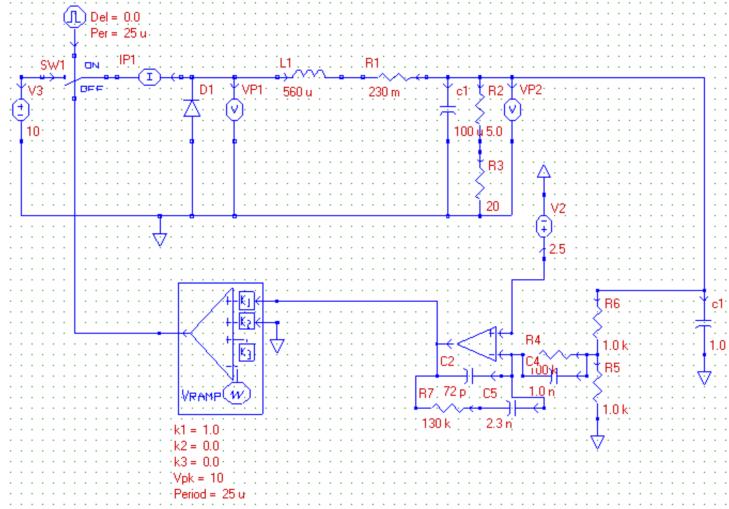


Figure 10: PECS schematic for voltage step response

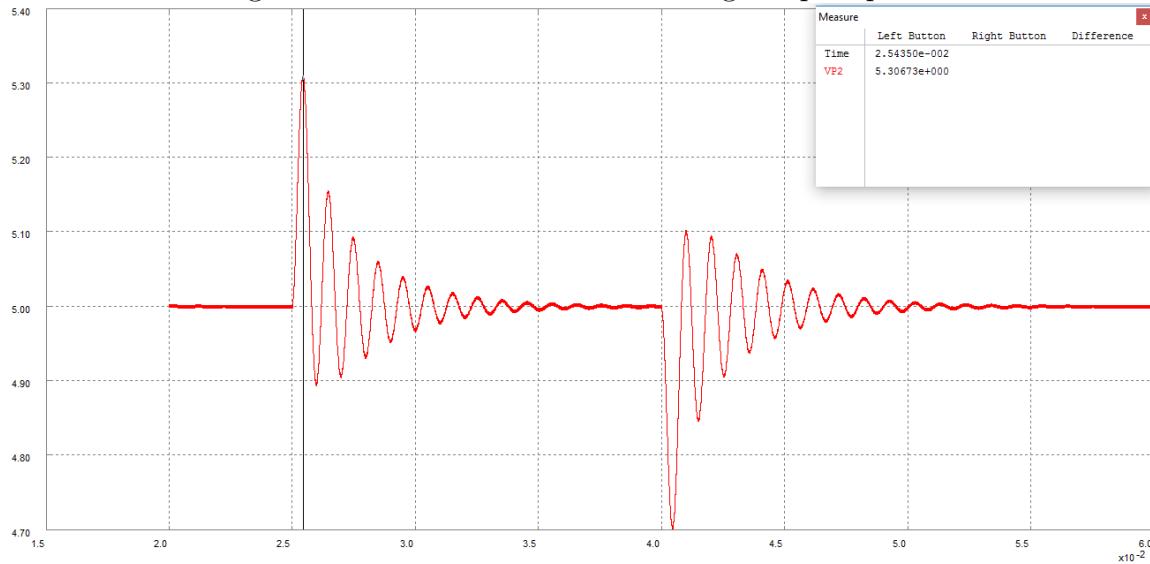


Figure 11: PECS voltage step response

| ΔV | SSE |
|------------|--------|
| 1V | .00005 |

Task 4b

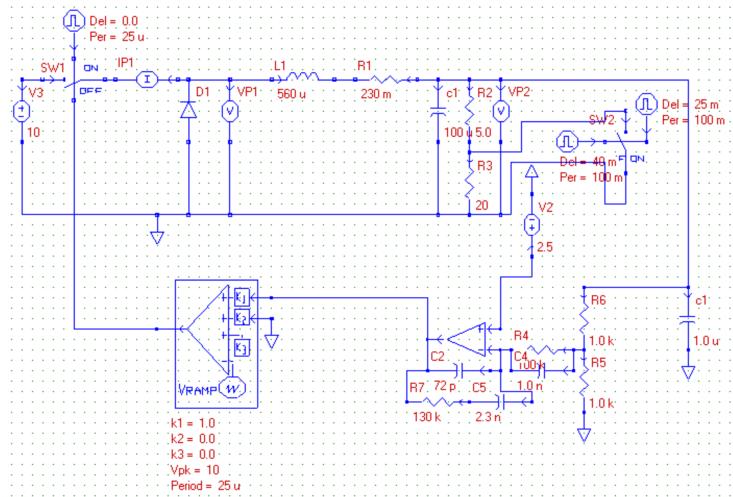


Figure 12: PECS Impedance step response

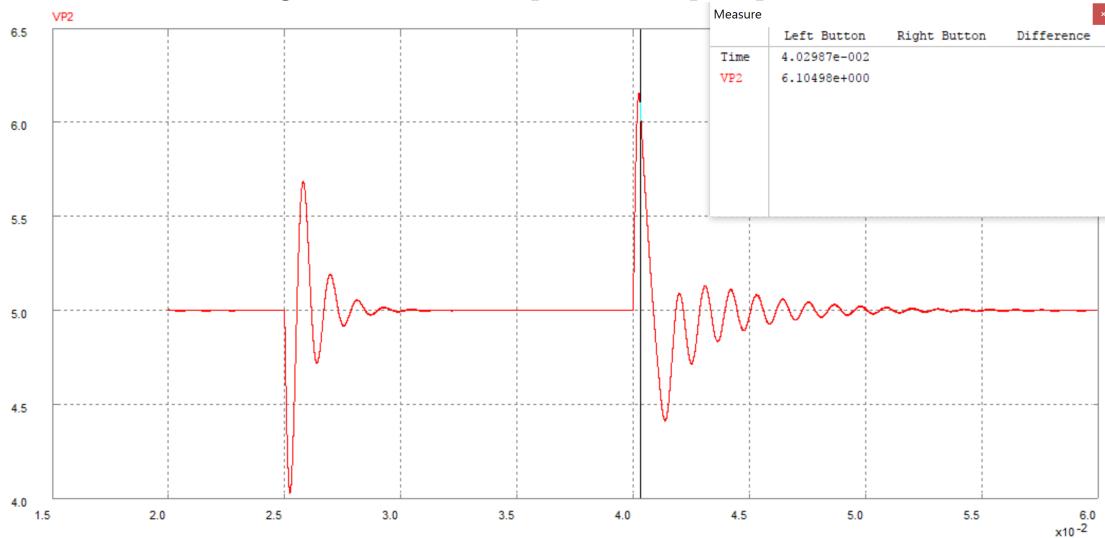


Figure 13: PECS Impedance step response

| ΔV | SSE |
|------------|-------|
| 2.1V | .0002 |

Circuit testing

Task 5b

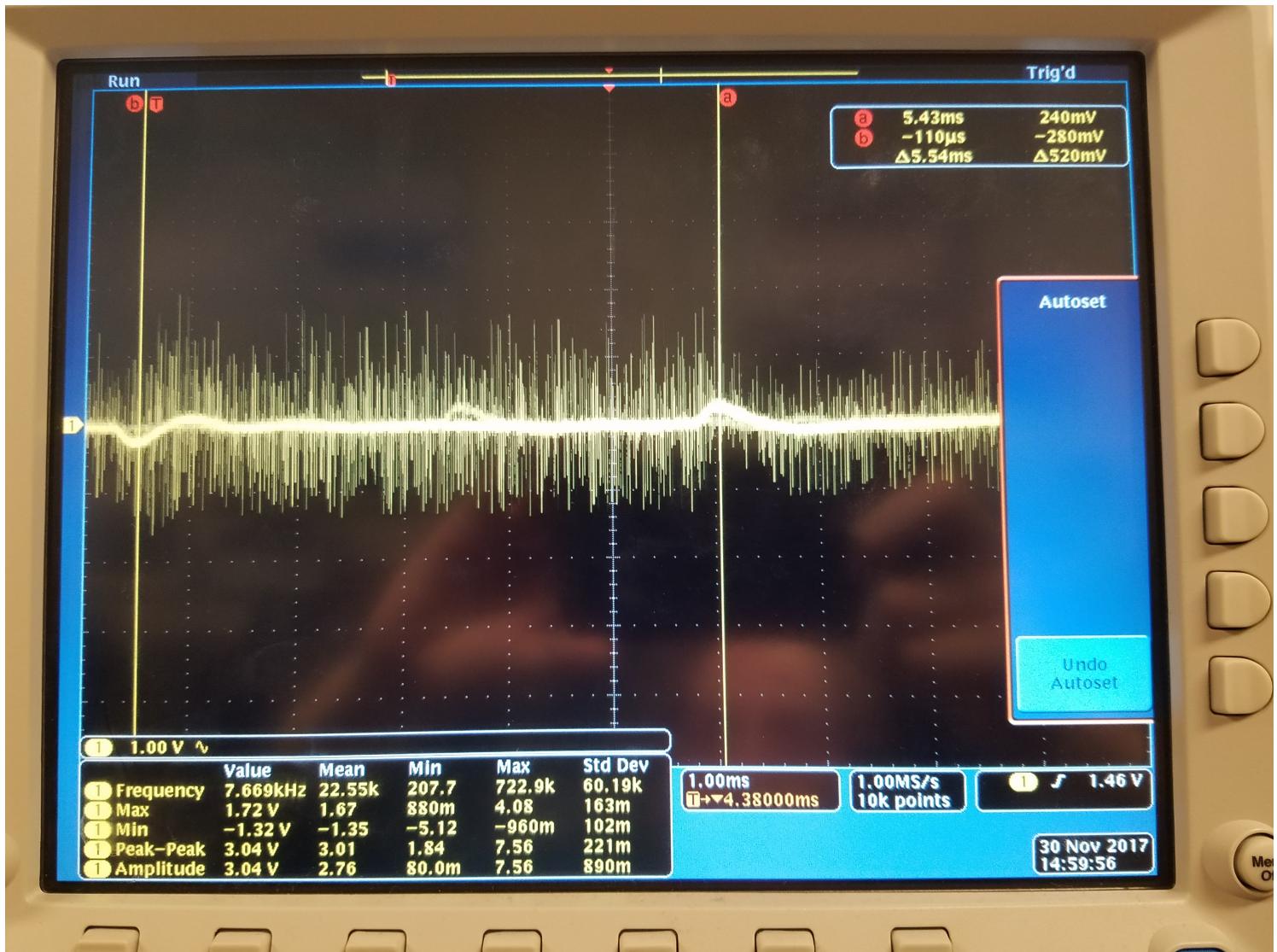


Figure 14: Impedance step response in real life

| ΔV | SSE |
|-------|------|
| 580mV | 20mV |

Task 6a

| | Phase Margin Φ in degrees | Unity Gain Crossover, f_c | Gain Margin G_m | Phase Crossover Frequency |
|------------|--------------------------------|-----------------------------|-------------------|---------------------------|
| Asymptotes | 45 | 5k | inf dB | inf Hz |
| Matlab | 50.8 | 5.09kHz | inf dB | inf Hz |

Task 6b

| | Openloop (Uncompensated) | Integral compensator | Integral + lead compensator. |
|----------------------------------|--------------------------|------------------------|---|
| Compensator transfer function | N/A | $\frac{1}{RC \cdot s}$ | $\frac{-\omega_I(1+\frac{s}{\omega_A})(1+\frac{s}{\omega_S})}{s(1+\frac{s}{\omega_p})}$ |
| Φ_{PM} in MATLAB | 15.6 | 89 | 50.8 |
| f_c MATLAB | 5.92kHz | 34Hz | 5.09kHz |
| i_{out} step ΔV LAB | 2.6V | 3.8V | 580mV |
| i_{out} step ΔV PECS | 2.89 | 2.47 | 2.1 |
| i_{out} step ΔV MATLAB | 3.4017 | 3.52 | .39V |
| i_{out} step SSE LAB | .16V | 0 | 20mV |
| i_{out} step SSE PECS | .17V | .01946 | .0002 |
| i_{out} step SSE MATLAB | .1838 | .0064 | $-1.11 \cdot 10^{-6}$ |
| v_g step ΔV PECS | 1.15 | 1.48V | 1 |
| v_g step ΔV MATLAB | 2.47 | 1.6 | .0387 |
| v_g step SSE PECS | .498 | .01823 | .00005 |
| v_g step SSE MATLAB | .9977 | .0099 | $8.83 \cdot 10^{-18}$ |